

How a DIODE works...

A DIODE is an “Electron gate” allowing electrons to travel in only one direction. A diode will allow POSITIVE (+) voltage to travel from the ANODE (+) through to the CATHODE (-). It WILL NOT allow POSITIVE (+) voltage to travel from the CATHODE (-) to the ANODE (+).

IMPORTANT REMINDER: The BAND on a DIODE marks the CATHODE or NEGATIVE (-) side of the DIODE.



When working with a NEGATIVE (-) signal, the DIODE works in reverse. A NEGATIVE signal will travel from the CATHODE (-) to the ANODE (+), BUT WILL NOT travel from the ANODE (+) to the CATHODE (-).

DIODES ARE NECESSARY IN THE FOLLOWING COMMON APPLICATIONS:

1. Connecting (2) two sets of SWITCH OUTPUTS (the switch outputs are the output wires or trigger wires from a shock sensor or a hood pin switch that triggers the alarm to sound) to the same TRIGGER INPUT wire (the trigger input wire is the MAJOR or MINOR NEGATIVE (-) input wires usually the GREEN and YELLOW wires on the alarm).
2. Sending (2) two different circuit control pulses while keeping them isolated from each other.
3. Preventing feedback through the windings of a relay coil.

IMPORTANT REMINDER: the most common diode is part number 1N4001 to 1N4004 they are 1-amp general-purpose diodes, use the appropriate amperage rating.